

 [smolao](#) / [Digital-electronics-1](#)

<> Code

! Issues

🔗 Pull requests

▶ Actions

📁 Projects

📖 Wiki

🛡 Security

🔑 main ▾

...

[Digital-electronics-1](#) / [Labs](#) / [03-vivado](#) / README3.md

Ondřej Smola splnil

🕒 History

👤 0 contributors

Raw

Blame



60 lines (41 sloc) | 1.67 KB

3rd task - Vivado (Ondřej Smola - 217628)

1st Preparation task

2nd Two-bit wide 4-to-1 multiplexer

Listing of VHDL architecture from source file

```
architecture Behavioral of mux_2bit_4to1 is
begin
    f_o <= a_i when (sel_i = "00") else
           b_i when (sel_i = "01") else
           c_i when (sel_i = "10") else
           d_i;

    -- WRITE "GREATER" AND "EQUALS" ASSIGNMENTS HERE

end architecture Behavioral;
```

Listing od VHDL stimulus process from testbench file

```
p_stimulus : process
begin
    -- Report a note at the beginning of stimulus process
    report "Stimulus process started" severity note;

    -- First test values
    s_d <= "00"; s_c <= "00"; s_b <= "00"; s_a <= "00";
    s_sel <= "00"; wait for 100 ns;

    s_d <= "10"; s_c <= "01"; s_b <= "01"; s_a <= "00";
    s_sel <= "00"; wait for 100 ns;


    s_d <= "10"; s_c <= "01"; s_b <= "01"; s_a <= "11";
    s_sel <= "00"; wait for 100 ns;

    s_d <= "10"; s_c <= "01"; s_b <= "01"; s_a <= "00";
    s_sel <= "01"; wait for 100 ns;

    s_d <= "10"; s_c <= "01"; s_b <= "11"; s_a <= "00";
    s_sel <= "01"; wait for 100 ns;
    -- WRITE OTHER TEST CASES HERE

    -- Report a note at the end of stimulus process
    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;
```

Screenshot with simulated time waweforms

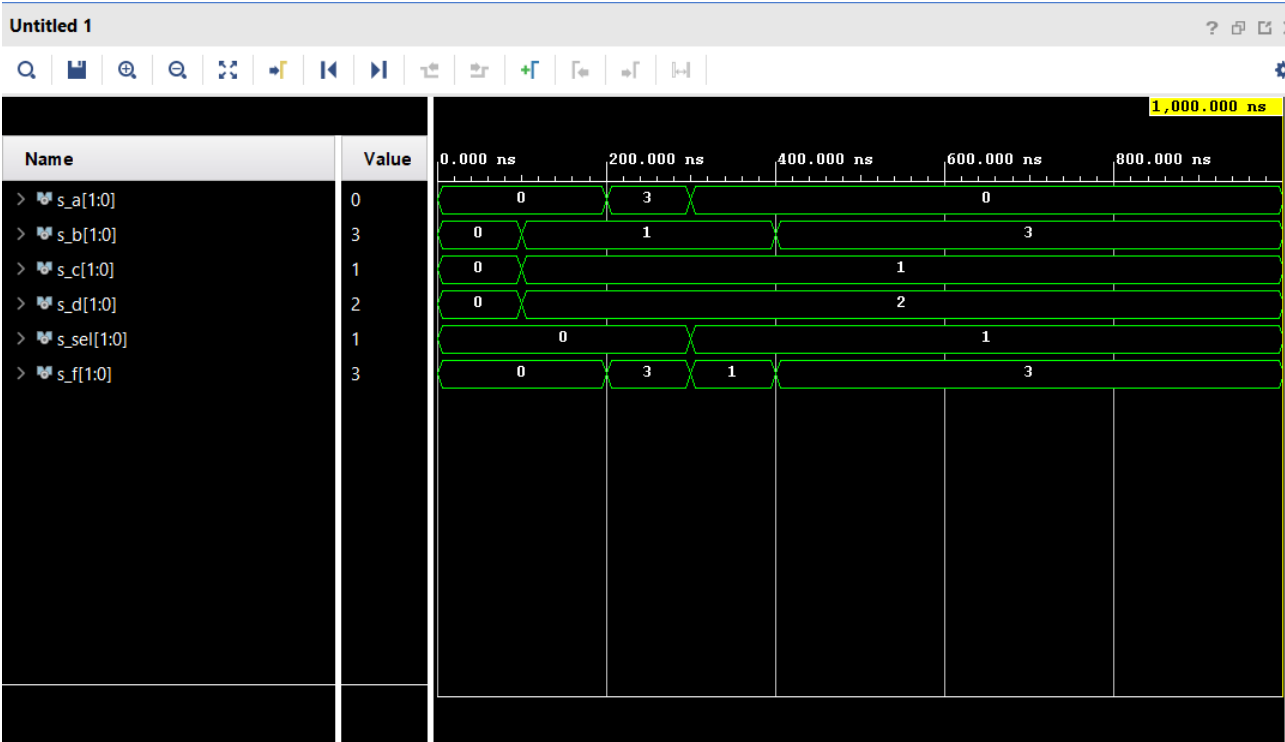

3rd Task - Link to my README file with Vivado Tutorial

[My Vivado tutorial](#)